Declaration of authorship

Krzysztof Rudnicki Student Number: 307585

May 12, 2022

I declare that this piece of work which is the basis for recognition of achieving learning outcomes in the (Microprocessor Systems) EMISY course was completed on my own

EMISY Project 21 Portable Compass

Krzysztof Rudnicki, 307585

June 7, 2022

1 Analysis of the project

1.1 Discussion of project requirements

We need to create a simple portable compass circuit It should:

- Use energy-saving power modes of microcontroller
- Be battery powered
- Be portable (cellphone/wrist watch)
- Communicate using graphical OLED display and two buttons keyboard

1.2 Discussion of solution


In my solution I focused on picking components based on firstly low power consumption, then size, then simplicity, whenever I could I tried to do everything as proposed in the component data sheet.


For the schematic itself I needed power saving microcontroller, oled display, battery, voltage regulator that works well with batteries and digital compass.

2 Detailed circuit diagram

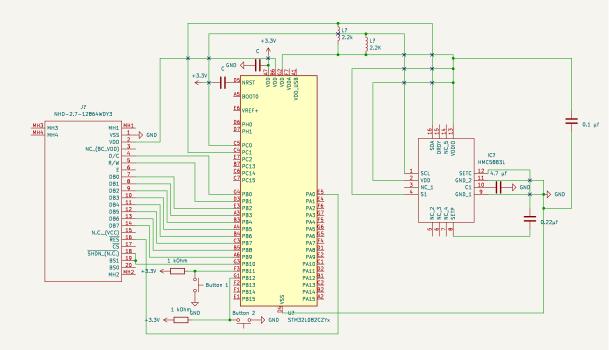2.1 Diagram itself

(Diagram is in pdf format so feel free to zoom in if something is not clearly visible)



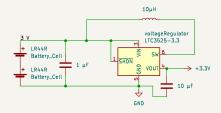

/

2.2 Diagram description

Voltage regulator schematic is done one to one on how it was done in voltage regulator schematic in case of two battery cells

Digital compass also was connected exactly as specified in datasheet

For OLED I based on the pin descriptions from datasheet and on common patterns of connecting peripherals

Microcontroller itself was pretty straightforward with classic VDD, VSS and Reset pin conections $\,$

For buttons I used pull up resistors

2.3 Components

2.3.1 Microcontroller

I decided to use STM32L082CZ from STM32L0 line

Relatively small Up to $10 \text{ mm} \times 10 \text{ mm}$ dimensions, compared to apple watch display of 34 mm by 40 mm for smaller version. [1] 111th page

Square It is shaped in a square which also simplifies portability [1] 111th page

Power saving STM32L0 line was designed specifically for low power consumption with power consumption as low as 0.29 μ A in Standby mode [1] 1st page

Consumer devices This microcontroller comes from STM32LOx2 line prepared to be used in consumer devices [2]

Ease of use USB compatible microcontroller and dedicaded debug port allows for swift code creation. [1] 1st page

2.3.2 All other components

Oled display For OLED display I decided to go with NHD-2.7-12864WDY3. It was an OLED display found on mouser webpage with lowest operating supply current of 180 uA, supply voltage compatible wit microcontroller (3.3 V) and datasheet not in japanese. [3]

Digital compass For the compass I used HMC5883L with compatible voltage, low power consumption of 100 μ A, compatiblity with battery powered applications according to datasheet and small size

Battery For the battery I choose 2x LR44R series battery, with output voltage of 1.5 V compatible with voltage regulator (3 V in series), compatible battery chemistry of Alkaline, 150 mAh capacity for single battery and compact coin cell shape. [5]

Voltage Regulator For voltage regulator I choose LTC3525-3.3 with high 95 % efficiency, desirable output voltage of 3.3 V, low profile and tiny package, it is also available in kicad by default [6]

3 Draft of the microcontroller firmware

3.1 Block diagram

Figure 1: Start algorithm

Initialize

Wait for all components to start

Begin Microprocessor system work

Request shutdown

Turn off everything

Return


Figure 2: Main loop

 ${\bf Begin\ Microprocessor\ system\ work}$

 ${\it buttonClicked} = 0$

Button Interrupts

Infinite loop

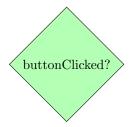

Do a single measurement

Stop mode without RTC

buttonClicked = 0

Wait for interrupt

Infinite loop

Request shutdown

Figure 3: Single measurement algorithm

Do a single measurement

Take measurement from magnetometer

Output measurment to display

Finish measurement

3.2 Description of the algorithm

References

- [1] STM32LO82CZ datasheet
- [2] Consumer Device STM32LOx2 Line
- [3] OLED datasheet
- [4] Magnetometer datasheet
- [5] Battery
- [6] Voltage regulator